

[Total No. of Questions: 09]  
Uni. Roll No. ....

[Total No. of Pages: 03]

Program: B.Tech. (Batch 2018 onward)  
Semester: 3rd  
Name of Subject: Analog Electronics  
Subject Code: PCEE-102  
Paper ID: 16065

Scientific calculator is Allowed  
Detail of allowed codes/charts/tables etc. NIL  
Time Allowed: 03 Hours

Max. Marks: 60

**NOTE:**

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

**Part – A**

[Marks: 02 each]

**Q1.**

- a) Define a P-N junction diode. What are two different types of charge carriers in P-N junction diode?
- b) Draw the schematic symbol of a BJT and label its terminals. Explain the I-V characteristics of a BJT in the active region.
- c) Describe the operation of a MOSFET as a switch in the cut off and saturation regions.
- d) Define a differential amplifier and explain its significance in analog signal processing. Discuss the advantages of using a differential amplifier in applications such as amplification and noise rejection.
- e) An ideal op-amp is connected in an inverting amplifier configuration with a gain of -10. If the input voltage is 2 V, calculate the output voltage.
- f) Design an op-amp integrator circuit with a time constant of 0.1 seconds. If the input voltage is a square wave with a frequency of 1 kHz and an amplitude of 2 V, calculate the output voltage waveform.

**Part – B**

[Marks: 04 each]

- Q2. Describe the working principle of a half-wave rectifier. Compare and contrast the advantages and disadvantages of a half-wave rectifier and a full-wave rectifier.
- Q3. Define the small-signal model of a BJT and explain its significance in amplifier design. Derive the expression for the voltage gain of a common-emitter amplifier using the small-signal model.
- Q4. Define the ideal characteristics of an operational amplifier. Explain the implications of infinite open-loop gain, infinite input impedance, zero output impedance, and zero offset voltage in an ideal op-amp.
- Q5. A power amplifier has a supply voltage of 24 V and a load resistance of 8 ohms. If the amplifier is designed to deliver a maximum power of 50 W, calculate the peak output voltage and the maximum current delivered to the load.
- Q6. Design a biasing circuit for a common-source MOSFET amplifier using a resistor and a voltage divider network. The MOSFET has a threshold voltage of 2 V and requires a drain current of 2 mA. The supply voltage is 10 V. Calculate the resistor values for proper biasing.
- Q7. a) Compare and contrast the inverting and non-inverting amplifier configurations.  
b) Derive the voltage gain equations for both inverting and non-inverting amplifiers.
- Q8. Derive the small-signal equivalent circuit of a common-emitter amplifier. Calculate the voltage gain, input impedance, and output impedance of the derived small-signal model. Discuss the importance of coupling and bypass capacitors in small-signal amplifier circuits.

OR

MORNING

11 MAY 2023

Explain the operating principle of a Zener diode and its unique characteristic in the reverse-biased region. A Zener diode has a breakdown voltage of 5.6 V. If a current of 10 mA flows through the diode when it is reverse biased, calculate the dynamic resistance of the Zener diode.

- Q9. Explain the concept of lead and lag compensation in control systems. Derive the transfer function of a lead compensator using an op-amp. Discuss the advantages and limitations of lead and lag compensators.

OR

Derive the small-signal equivalent circuit of a direct-coupled multi-stage amplifier. Calculate the voltage gain, input impedance, and output impedance of the derived small-signal model. Discuss the advantages and disadvantages of using direct coupling in multi-stage amplifiers.

\*\*\*\*\*